


Pirate Shift

Based on Deluxe Pirate Pitch by Mid-Fi Electronics.

Chorus/Vibrato

By PCB Guitar Mania

[Project link](#)

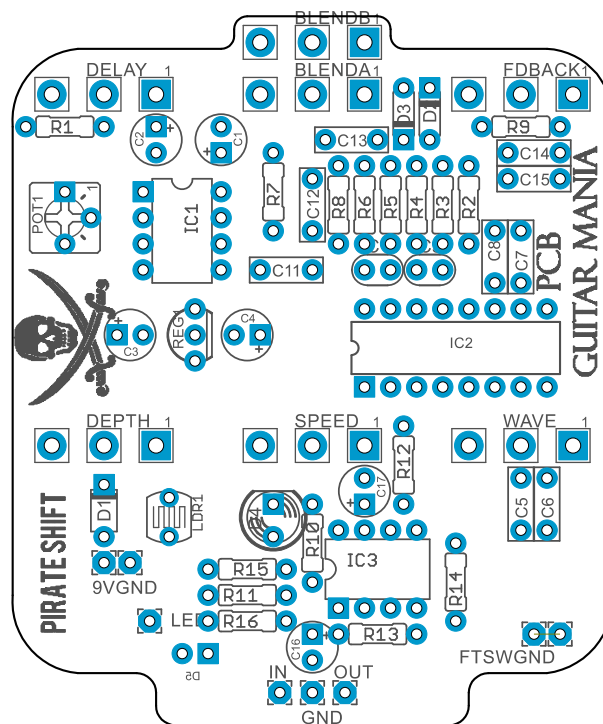

The Pirate Shift is a Chorus/Vibrato merged with a PT2399 based delay. It also has the ability to modulate over an octave as well as control the waveform of the modulator, giving you a huge range of tonal options. It works from a standard chorus to a crazy modulation device.

- Ready to be wired as True Bypass.
- Tight design to fit in a 125B Enclosure.
- Internal trimpot to regulate the Input.

BOM

C1	47UF	R1	1k
C2	47UF	R2	22k
C3	47uf	R3	10k
C4	47uf	R4	22k
C5	100nf	R5	22k
C6	100nf	R6	10k
C7	100nf	R7	100k
C8	100nf	R8	100k
C9	1nf	R9	15k
C10	1nf	R10	10k
C11	10nf	R11	10k
C12	100nf	R12	1k
C13	100nf	R13	47k
C14	100nf	R14	100k
C15	100nf	R15	10k
C16	1uf	R16	10k
C17	47uf		
		SPEED	B1m
D1	1N4001	WAVE	B1k
D2	1n4148	DELAY	B100k
D3	1n4148	DEPTH	B100k
D4	LED5MM*	FDBACK	B50k
D5	LED3MM	BLEND	B50k Dual gang (stereo)
		Trimmer	100K
IC1	LM386		
IC2	Pt-2399	REG1	Lm78L05**
IC3	JRC 4558	LDR1	Photo resistor*

Photo resistor/ Photo coupler *

The project features two different alternatives here, the stock version using a **VTL5C2** photo coupler, or to build your own with a 5mm led facing a photo resistor like the **KE-10720** inside a piece of heat-shrink tube. The home-made alternative brings you the opportunity to customize much more the LFO of the effect just by changing the led color, brightness or even the distance in between the led and the photo resistor.

Lm78L05**

It's recommended, in order keep the project tidy, to get this part on a To-92 package (the one that looks like a standard transistor). The TO-220 will work great also, but some people might find it to big.

Shopping list

Resistors

1	47k	R13
3	22k	R2, R4, R5
1	15k	R9
2	1k	R1, R12
6	10k	R3, R6, R10, R11, R15, R16
3	100k	R7, R8, R14
1	5mm Photo resistor	LDR1

Capacitors

8	100nf	C5, C6, C7, C8, C12, C13, C14, C15
2	1nf	C9, C10
1	10nf	C11

Electrolytic

1	1uf	C16
2	47UF	C1, C2
3	47uf	C3, C4, C17

Semiconductors

1	LM386	IC1
1	JRC 4558D	IC3
1	Pt-2399	IC2
1	LM78L05**	REG1

Pots

1	100K	POT1
2	B100k	DELAY, DEPTH
1	B1k	WAVE
1	B1m	SPEED
1	B50k	FDBACK
1	B50k Stereo	BLEND A, BLEND B,

Diodes

2	1n4148	D2, D3
1	1n4001	D1
1	Led 3mm	D5
1	Led 5mm*	D4

Photocoupler


1	VTL5C2*	
---	---------	--

General Building notes

To populate the PCB it's recommended to follow this order.

1. Resistors & diodes
2. IC Sockets (set up the proper IC at last)
3. Capacitors, starting with the smaller ones and the ceramic ones.
4. Electrolytic capacitors (always check the polarity)
5. Transistors
6. Wires
7. Potentiometers
8. Off board wiring

Off Board Wiring

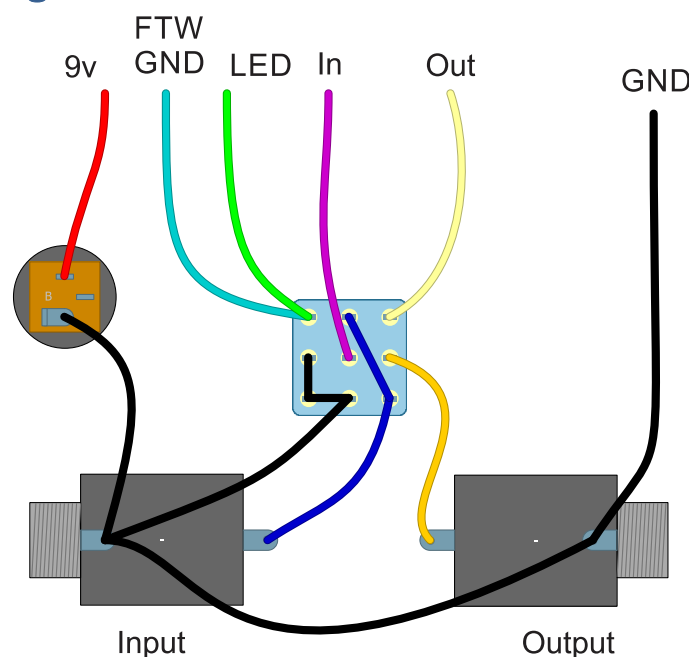

There are two wires going from the control pin of the 3pdt to the board. One is to control the status LED, and the other one is to control the internal LED, the one that controls de modulation and the photo resistor.

Drilling the enclosure

This Project has been planned to fit into a 125B enclosure type (122x67x35mm approx.)

Check the Attached "Drilling templates" to drill the box properly. The files are on Scale 1:1, ready to print in a A4 page.

Schematic

