Ojo Diablo!

Based on: Amount of parts: Enclosure type:

Okko Diablo+ High, total 52 components 1590bb

Effect type: Technology: Get your board at:

Overdrive Jfet Cascade Stages Ojo Diablo!


Build difficult: Power consumption: Get your kit at:

Advanced 20mA (9v) <u>Das Musikding (Europe)</u>

Project overview:

The Ojo Diablo! Is a versatile low to medium gain overdrive with an exceptionally dynamic response. It preserves the character of your instruments and is very sensitive to your playing technique.

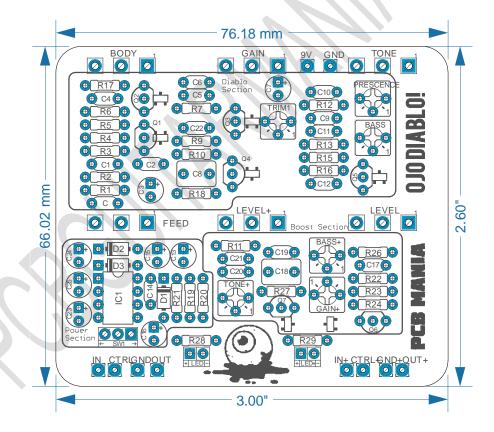Thanks to the effective and musical controls, the Diablo works equally well with any kind of guitar, amp or playing style.



Index

- 1. Project overview
- 2. Index, Introduction & Controls
- 3. Bills of Materials, BOM
- 4. Shopping Lists
- 5. Components Recommendations

- 6. Build Notes
- 7. Schematic
- 8. Wiring Diagram
- 9. Drill Template
- 10. Licensing and Usage

Introduction

Definitely one of the most complete overdrives there's out there! Featuring six potentiometers, six internal trimmers and a headroom toggle we can assure that the Ojo Diablo! Is by far one of the most versatile overdrives ever built.

Controls

External Controls

- Feed: Pre-gain control, adjust the amount of bass in the input signal for a tight and transparent sound even with the fattest neck pickups
- Body: Takes effect on lower mids and compression. To the LEFT tight and open, to the RIGHT Fat and singing.
- Tone: Set your tone preferences all the way from dark to bright. You can further fine-tune its response with the internal trim pots
- Gain: Controls the intensity of distortion. Set it to the desired level of distortion and roll back the guitar volume for cleaner tones.
- Level: Overall volume level of the pedal
- Level+: Controls the second gain settings. This control works in addition with the gain control, so if Gain is already on maximum, engaging the LEVEL + won't give you any more distortion, just a slight fattening of the sound.
- Headroom Switch: Activates the internal Voltage doubler.

Internal Controls

- Presence: Controls High frequencies of the main section.
- Bass: Affects lower mids and Bass frequencies of the main section.
- TRIM1: Originally a 100r resistor, this trimmer allows you to regulate the gain of Q3
- Tone+: Set the Tone response of the second section
- Bass+: Set the Bass response of the second section
- Gain+: This trimmer allows you to do the fine-tuning of the second section gain.

Bill of materials

Parts Value R1 10k R2 1m R3 1m R4 47k R5 1k R6 1k R7 10k R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R25 1k R27 470k R28 2k7-4k7 R29 2k7-4k7	Resistors		
R2 1m R3 1m R4 47k R5 1k R6 1k R7 10k R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	Parts	Value	
R3 1m R4 47k R5 1k R6 1k R7 10k R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R1	10k	
R4 47k R5 1k R6 1k R7 10k R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R2	1m	
R5 1k R6 1k R7 10k R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R3	1m	
R6 1k R7 10k R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R4	47k	
R7 10k R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R5	1k	
R9 1k R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R6	1k	
R10 47k R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R7	10k	
R11 1m R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R9	1k	
R12 39k R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R10	47k	
R13 43k R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R11	1m	
R15 1m R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R12	39k	
R16 3k3 R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R13	43k	
R17 470k R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R15	1m	
R18 470k R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R16	3k3	
R19 10k R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R17	470k	
R20 10k R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R18	470k	
R21 100E R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R19	10k	
R22 1m R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R20	10k	
R23 10k R24 1m R26 1k R27 470k R28 2k7-4k7	R21	100E	
R24 1m R26 1k R27 470k R28 2k7-4k7	R22	1m	
R26 1k R27 470k R28 2k7-4k7	R23	10k	
R27 470k R28 2k7-4k7	R24	1m	
R28 2k7-4k7	R26	1k	
	R27	470k	
R29 2k7-4k7	R28	2k7-4k7	
	R29	2k7-4k7	

Capacitors		
Parts	Value	
С	1n	
C1	3n3	
C2	470p	
C3	10uf	
C4	47n	
C5	100n	
C6	470p	
C7	47uf	
C8	1u NP	
C9	3n3	
C10	8n2	
C11	100n	
C12	100n	
C13	47uf	
C14	10n	
C15	100uf	
C16	100uf	
C17	100n	
C18	1u NP	
C19	10n	
C20	100n	
C21	47n	
C22	150pf**	
C23	47uf	
C24	47uf	
C25	47uf	

pots		
Parts	Value	
TONE	100k B	
FEED	1M A	
GAIN	500K A	
LEVEL	100K A	
LEVEL+	100K A	
BODY	1M B	

TRIMMERs		
Parts	Value	
TONE+	100k	
TRIM1*	1K*	
GAIN+	5k	
BASS	100k	
BASS+	100K	
PRESCENCE	100k	

Switches	
Parts	Value
SW1	SPDT on-on

Transistors		
Parts	Value	
Q1	J201	
Q2	J201	
Q3	J201	
Q4	J201	
Q5	J201	
Q6	J201	
Q7	J201	

Semiconductor		
Parts	Value	
D1	1n4001	
D2	1n4001	
D3	1n4001	
IC1	MAX 1044	
LED	3mm LED	
LED+	ED+ 3mm LED	

Shopping list

Resistors		
Qty	Value	Parts
5	10k	R1, R7, R19, R20, R23
1	39k	R12
1	43k	R13
1	3k3	R16
3	470k	R17, R18, R27
6	1m	R2, R3, R11, R15, R22,
		R24
1	100r	R21
2	2k7-4k7	R28, R29
2	47k	R4, R10
4	1k	R5, R6, R9, R26

Capacitors		
Qty	Value	Parts
1	1n	С
2	3n3	C1, C9
1	8n2	C10
2	10n	C14, C19
2	100uf	C15, C16
2	470p	C2, C6
1	150p	C22
1	10u	C3
2	47n	C4, C21
5	100n	C5, C11, C12, C17, C20
5	47uf	C7, C13, C23, C24, C25
2	1u NP	C8, C18

Trimpots		
Qty	Value	Parts
4	100k	BASS, PRESCENCE, TONE+, BASS+
1	5k	GAIN+
1	1K	TRIM1

Potentiometer		
Qty	Value	Parts
1	100k B	TONE
1	1M A	FEED
1	500K A	GAIN
1	1M B	BODY
2	100K A	LEVEL, LEVEL+

Semiconductors		
Qty	Value	Parts
1	MAX 1044	IC1
2	LED 3mm	LED, LED+
3	1n4001	D1, D2, D3
7	J201	Q1, Q2, Q3, Q4, Q5, Q6, Q7

Switches		
Qty	Value	Parts
1	SPTDT ON-ON	SW1
1	3PDT Stomp food	-

Components Recommendations

Always ensure the max tolerance of your **electrolytic capacitors** is over 25v.

This board has been tested using Film box capacitors for most of the values over 1nf, and ceramics discs for the ones under 1nf. However, high quality components such as Wima's Capacitors and Panasonic's electrolytics can deliver a better performance.

All the resistors used for testing this project are 1/4W Metal Film.

The BOM and Shopping list are exclusively regarding this project. It doesn't include all the hardware like the 3PDT bypass switch, audio/dc jacks, enclosure, etc.

The Transistors JFET J201 are the heart of this build. Make sure to get high quality ones from trusted vendors and not cheap Asian counterfeits! I strongly recommend the use of SMD transistors as they are much more reliable quality wise.

TRIM1*: This is an add on over the original 100r resistor in order to have a better control of the total amount of gain on the unit, especially if you feel to experiment with other JFET such as 2n5457. If you want to stick to the traditional version just place a 100r in between the pads.

C22** is not present on the original unit, however is an interesting add-on to keep the unwanted noises down.


Build Notes

If this is one of your first projects I recommend you to take a look on our Pedal Building Guide

For a successful and tidy build it's recommended the following order:

- 1. Resistors & diodes
- 2. Capacitors, starting with the smaller ones and the ceramic ones.
- 3. Electrolytic capacitors (always check the polarity)
- 4. Transistors
- 5. Wires
- 6. Potentiometers and switches
- 7. Off board wiring

Schematic

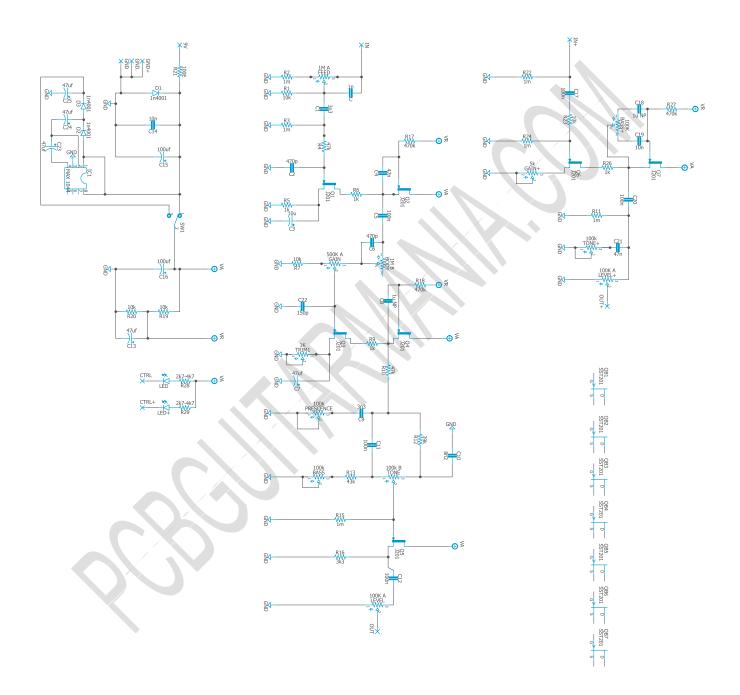


Wiring Diagram

All our projects include a free 3PDT Board to make the wiring easier and tidier. Also all of our PCBs feature the status LED on board.

The pad named "Ctrl" or "LED" is the one that controls the status of the led, wire it to the "LED "pad on the 3PDT board, or in control slug of your 3PDT.

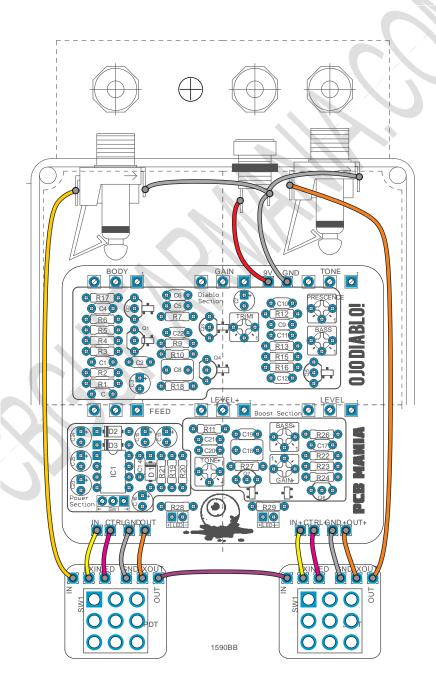You can take a look on the following diagram to understand the general connections. The headroom switch isn't present on the following diagram. To wire it properly just extend three wires from the pads in the board to the Switch slugs. On my opinion the best place for the switch is in between the audio Input and the DC Jack, just as on the original Okko Diablo +



Drill Template

This Project has been planned to fit into a 1590BB enclosure type.

Check the Attached "Drilling templates" to drill the box properly. The files are on Scale 1:1, ready to print in an A4 page.

Licensing and Usage

We really appreciate your trust and support buying this PCB, as well as your will to dive into the DIY electronics world. That's why for us is really important that you can make this project work properly and to enjoy not only the building process, but also to experiment and play with it on your rig.

We try to reply to every question we receive on our email or in our social media, but we try to encourage all our customers to join our <u>PCB Guitar Mania – Builders Group</u> on Facebook, in order to post all your doubts, issues, suggestions or request, as well to share your builds and have some feedback from us and other fellow builders!

All of our projects have been tested following this same guide on their standard configurations. Although, not all of the variations and mods have necessarily been tested. These are suggestions based on the schematic analysis, and on the experiences and opinions of others. Feel free to share with us your opinions and suggestions regarding the mods your own personal experimentation.

These boards may be used for commercial endeavors in any quantity unless specifically noted. No attribution is necessary, though accreditation or a link back is always greatly appreciated.

If you are a builder planning to make your own run of pedals we also offer the service of custom made boards with your brand and logo, design according your specifications.

The only usage restrictions are that, first, you cannot resell the PCB as part of a kit without prior arrangement with us, and second, you cannot scratch off the silk screen, or other way of trying to hide our logos and the source of the PCBs. Like it's written above, if you want to have your own designs, with your brand and logo we could certainly reach an agreement.

Follow us on <u>Instagram</u> and <u>Facebook</u> to stay in tune with the latest projects!