

Tremolo Factory

Based on:

Zvex Seek Trem

Effect type:

Complex tremolo effect

Build difficult:

Intermediate

Number of parts:

Average, total 57 components

Technology:

Vactrol / Photoresistor

Power consumption:

9V

Enclosure type:

1590bb

Get your board at:


[Tremolo Factory](#)

Get your kit at:

[Das Musikding \(Europe\)](#)

Project overview:

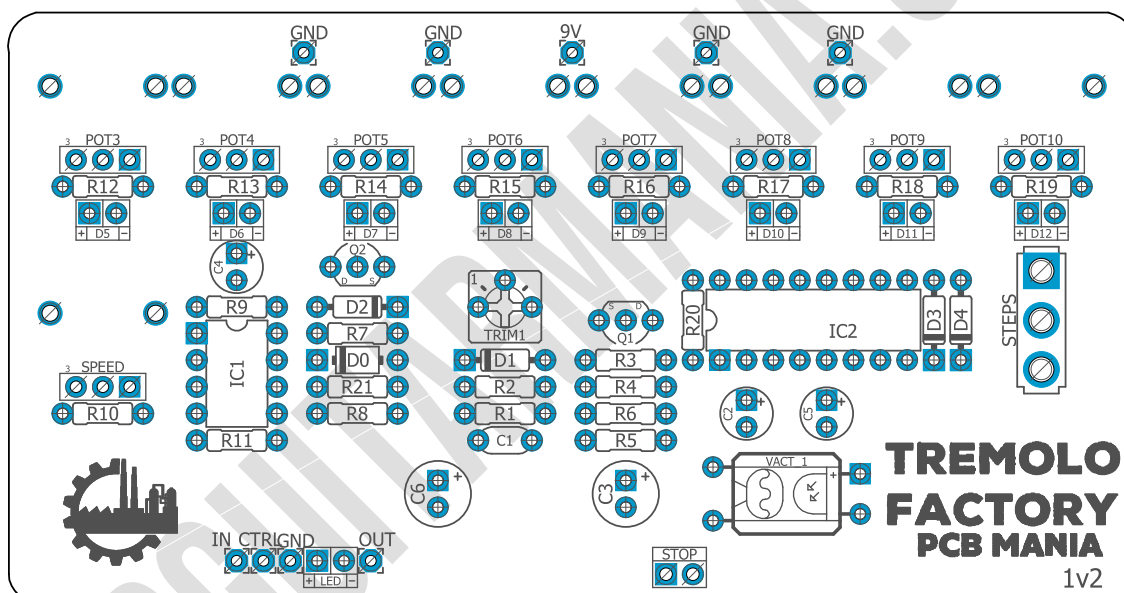Inspired by Zvex Seek Trem, the Tremolo Factory Rhythmic has all its well-oiled machinery ready to produce a ton of tremolos effects with complex patterns.



Index

- | | |
|-----------------------------------|--|
| 1. Project overview | 5. Schematic |
| 2. Index, Introduction & Controls | 6. Components, Build Notes, Wiring Diagram |
| 3. Bills of Materials, BOM | 7. Drill Template, Licensing and Usage |
| 4. Shopping Lists | |

Introduction

Are you up to this new industrial revolution? The purpose of this factory-board is to maximize the assembly of as many complex tremolos as possible. Now join us on this factory tour to observe the line production processes at work:

Via toggle, you can choose if either 4,6 or 8 potentiometers send an impulse to a decade counter that hits an optocoupler (or white clear LED and LDR - Easier to source) and then goes its way back to the Tremolo circuit. This awesomely unique and straightforward take allows you to manufacture your own patterns with a minimal amount of easy-to-source parts. The second momentary footswitch resets the pattern, so you're not starting in the middle of it when engaging.

For a circuit test, the LEDs need to be placed in the PCB, or you will not get any Tremolo going on. We recommend using at least one metal shaft 9mm pot for the speed control, or the PCB will be held in place only by the toggle. We tried using 3 metal shaft 9mm potentiometers in our build. Another thing to keep in mind is that these 9mm plastic shaft pots require precise drilling and should be soldered with everything in the enclosure to allow a smooth rotation.

Now that you have seen how the making process works is your time to build this industrial setup. Are you ready to have a workshop of unlimited tremolos mass production in your own house?

Controls

Each knob labeled "POT" controls different steps of the tremolo sequence.

- | | |
|--------|---------|
| • POT4 | • POT8 |
| • POT5 | • POT9 |
| • POT6 | • POT10 |
| • POT7 | • SPEED |

Switches

- Stop
- Steps

Bill of materials

| Resistors | |
|-----------|-------|
| Part | Value |
| R1 | 1m |
| R2 | 2m7 |
| R3 | 2m7 |
| R4 | 510r |
| R5 | 470r |
| R6 | 10k |
| R7 | 100k |
| R8 | 100k |
| R9 | 10k |
| R10 | 10k |
| R11 | 22k |
| R12 | 33k |
| R13 | 33k |
| R14 | 33k |
| R15 | 33k |
| R16 | 33k |
| R17 | 33k |
| R18 | 33k |
| R19 | 33k |
| R20 | 33k |
| R21 | 4k7 |

| Capacitors | |
|------------|-------|
| Part | Value |
| C1 | 100n |

| Electrolytics Capacitors | |
|--------------------------|-------|
| Part | Value |
| C2 | 10u |
| C3 | 100u |
| C4 | 1u |
| C5 | 1u |
| C6 | 220u |

| Potentiometers | |
|----------------|--------|
| Part | Value |
| POT3 | 100k B |
| POT4 | 100k B |
| POT5 | 100k B |
| POT6 | 100k B |
| POT7 | 100k B |
| POT8 | 100k B |
| POT9 | 100k B |
| POT10 | 100k B |
| SPEED | 100k B |

| Trimpots | |
|----------|-------|
| Part | Value |
| TRIM1 | 5k |

| IC | |
|------|----------|
| Part | Value |
| IC1 | TL072 |
| IC2 | CD4017BE |

| Transistors | |
|-------------|-------|
| Part | Value |
| Q1 | BS170 |
| Q2 | BS170 |

| Vactrol | |
|---------|--------|
| Part | Value |
| VACT_1 | vtl5c3 |

| Switches | |
|----------|---------------------|
| Part | Value |
| STOP | SPST |
| STEPS | SPST (On/Off/On) |

| Diodes | |
|--------|-------------|
| Part | Value |
| D0 | 1n5817 |
| D1 | 1n757a |
| D2 | 1n4148 |
| D3 | 1n4148 |
| D4 | 1n4148 |
| D5 | 3mm LED |
| D6 | 3mm LED |
| D7 | 3mm LED |
| D8 | 3mm LED |
| D9 | 3mm LED |
| D10 | 3mm LED |
| D11 | 3mm LED |
| D12 | 3mm LED |
| LED | 3mm Red LED |

Shopping list

| Resistors | | |
|-----------|-------|---|
| Qty | Value | Parts |
| 2 | 100k | R7, R8 |
| 3 | 10k | R6, R9, R10 |
| 1 | 1m | R1 |
| 1 | 22k | R11 |
| 2 | 2m7 | R2, R3 |
| 9 | 33k | R12, R13, R14, R15, R16, R17, R18, R19, R20 |
| 1 | 470r | R5 |
| 1 | 4k7 | R21 |
| 1 | 510r | R4 |

| Capacitors | | |
|------------|-------|-------|
| Qty | Value | Parts |
| 1 | 100n | C1 |

| Electrolytics Capacitors | | |
|--------------------------|-------|--------|
| Qty | Value | Parts |
| 2 | 100u | C3 |
| 1 | 10u | C2 |
| 2 | 1u | C4, C5 |
| 1 | 220u | C6 |

| Potentiometers | | |
|----------------|--------|--|
| Qty | Value | Parts |
| 9 | 100k B | POT3, POT4, POT5, POT6, POT7, POT8, POT9, POT10, SPEED |

| Trim pots | | |
|-----------|-------|-------|
| Qty | Value | Parts |
| 1 | 5k | TRIM1 |


| IC | | |
|-----|----------|-------|
| Qty | Value | Parts |
| 1 | CD4017BE | IC2 |
| 1 | TL072 | IC1 |

| Transistors | | |
|-------------|-------|--------|
| Qty | Value | Parts |
| 2 | BS170 | Q1, Q2 |

| Vactrol | | |
|---------|--------|--------|
| Qty | Value | Parts |
| 1 | vtl5c3 | VACT_1 |

| Switches | | |
|----------|------------------|-------|
| Qty | Value | Parts |
| 1 | SPST (On/Off/On) | STEPS |
| 1 | SPST | STOP |

| Diodes | | |
|--------|-------------|-----------------------------------|
| Qty | Value | Parts |
| 3 | 1n4148 | D2, D3, D4 |
| 1 | 1n5817 | D0 |
| 1 | 1n757a | D1 |
| 8 | 3mm LED | D5, D6, D7, D8, D9, D10, D11, D12 |
| 1 | 3mm Red LED | LED |

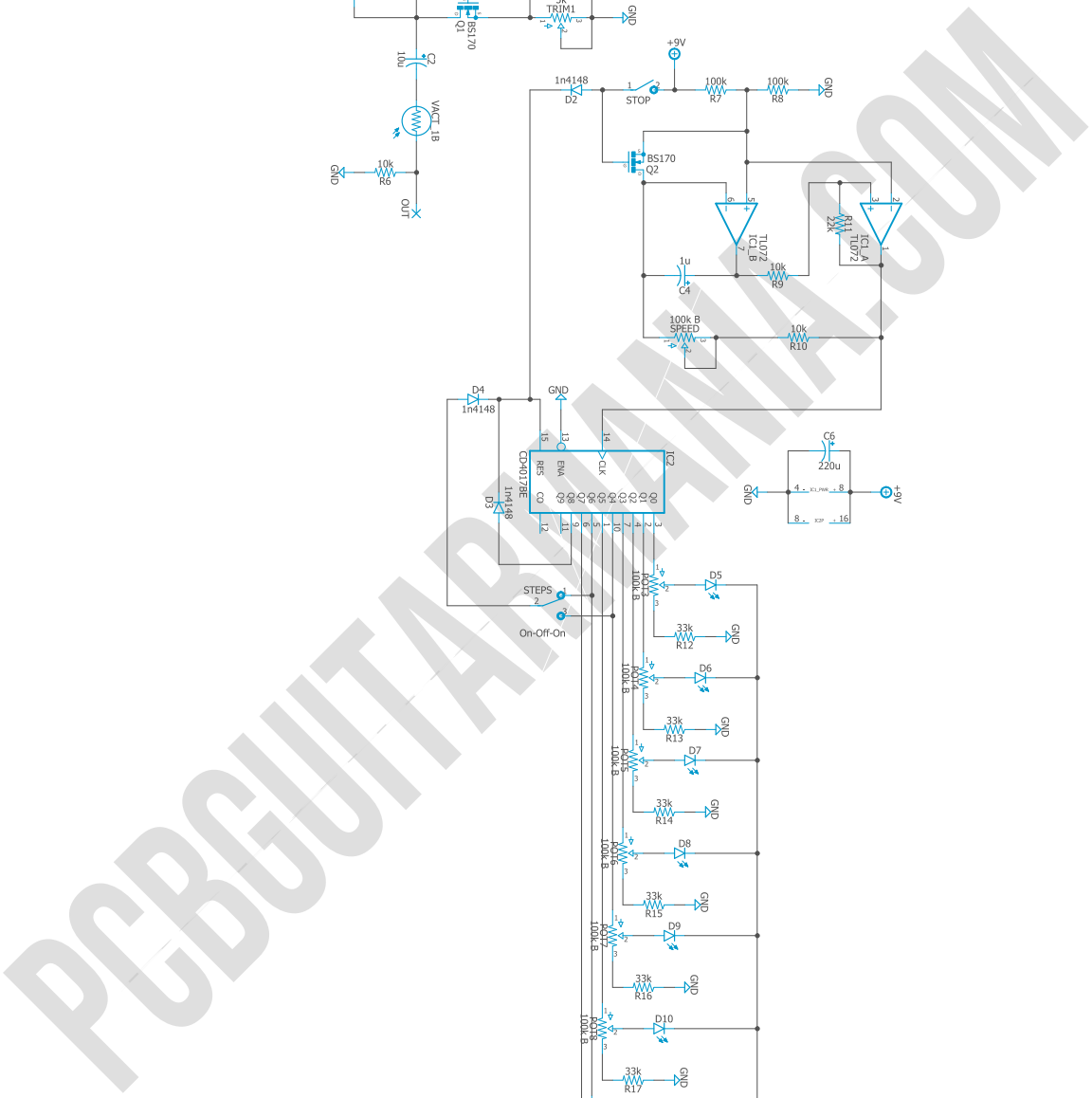

Components Recommendations

As many people like to experiment with some pedals with higher voltage, always ensure your **electrolytic capacitors'** max tolerance is over 25v.

This board has been tested using Film box capacitors for most of the values over 1nf and ceramics discs for those under 1nf. However, high-quality components such as Wima's Capacitors and Panasonic's electrolytics can deliver a better performance.

All the resistors used for testing this project are 1/4W Metal Film.

The BOM and Shopping list are exclusive regarding this project. It doesn't include all the hardware like the 3PDT bypass switch, audio/dc jacks, enclosure, etc.

Build Notes

If this is one of your first projects, I recommend you to take a look at our [Pedal Building Guide](#).

For a successful and tidy build, it's recommended the following order:

1. Resistors & diodes
2. Capacitors, starting with the smaller ones and the ceramic ones.
3. Electrolytic capacitors (always check the polarity)
4. Transistors
5. Wires
6. Potentiometers and switches
7. Off-board wiring

Wiring Diagram

All our projects include a free 3PDT Board to make the wiring easier and tidier. Also, all of our PCBs feature the status LED on board.

The pad named "Ctrl" or "LED" is the one that controls the status of the led; wire it to the "LED" pad on the 3PDT board or in the control slug of your 3PDT.

This board has been designed to match our EZ 3PDT PCB; check it [here](#) to access our [Pedal Wiring Guide](#).

Drill Template

This Project has been planned to fit into a 1590bb enclosure type.

Check the Attached “Drilling templates” to drill the box properly. The files are on Scale 1:1, ready to print on an A4 page.

Licensing and Usage

We really appreciate your trust and support in buying this PCB, as well as your will to dive into the DIY electronics world. For us, that's why you can make this project work properly and enjoy not only the building process but also experiment and play with it on your rig.

We try to reply to every question we receive on our email or our social media. Still, we try to encourage all our customers to join our [PCB Guitar Mania – Builders Group](#) on Facebook to post all your doubts, issues, suggestions, or requests, share your builds, and have some feedback from other fellow builders and us!

We tested all our projects following this same guide on their standard configurations. Although, not all of the variations and mods have necessarily been checked. These are suggestions based on the schematic analysis and the experiences and opinions of others. Feel free to share with us your views and recommendations regarding the mods your personal experimentation.

These boards may be used for commercial endeavors in any quantity unless expressly noted. No attribution is necessary, though accreditation or a link back is always much appreciated.

If you are a builder planning to make your own run of pedals, we also offer the service of custom-made boards with your brand and logo, design according to your specifications.

The only usage restrictions are that, first, you cannot resell the PCB as part of a kit without prior arrangement with us, and second, you cannot scratch off the silkscreen or other way of trying to hide our logos and the source of the PCBs. Like it's written above, if you want to have your designs with your brand and logo, we could undoubtedly reach an agreement.

Follow us on [Instagram](#) and [Facebook](#) to stay in tune with the latest projects!